

Date:10.04.2019

Student Names: Ahmet Emir KOCAĞA, Mete Han KURT

Student IDs: 2017400276,2016400339

Group ID: 1

Session ID: FF34

## CMPE 240 Experiment 5 Preliminary Work

1. State Register Inputs: Clk, D1, D0, Rst
2. State Register Outputs: N1, N0
3. Combinational Block Inputs: N1, N0, X
4. Combinational Block Outputs: Y1 , Y0, D1, D0
5. Obtain the truth table.

CURRENT STATE(N1,N0)	INPUTS (X)	NEXT STATE (D1,D0)	OUTPUTS (Y1, Y0)
00	0	10	10
00	1	00	11
01	0	10	10
01	1	00	11
10	0	10	10
10	1	11	10
11	0	10	11
11	1	11	01

6. Is this a Moore or Mealy Machine? (No explanation, only short answer)

Mealy

Date:10.04.2019

Student Names: Ahmet Emir KOCAĞA, Mete Han KURT

Student IDs: 2017400276,2016400339

Group ID: 1

Session ID: FF34

7. Draw the finite state machine.

